

Report: Experiment 2

Solutions Date: August 17, 2025


Name: Arnav Kapoor

Roll No: 23060



Title of Experiment: Familiarization with DC and AC sources

**Brief Description:** This experiment involves characterizing DC and AC sources using different resistors. V-I characteristics for each resistor are plotted for both DC and AC sources using data from exp-1.xlsx. LTspice simulations are performed for the same setups. The experiment also covers resistor color codes, calculation of resistance, and the concept of non-ohmic behavior.

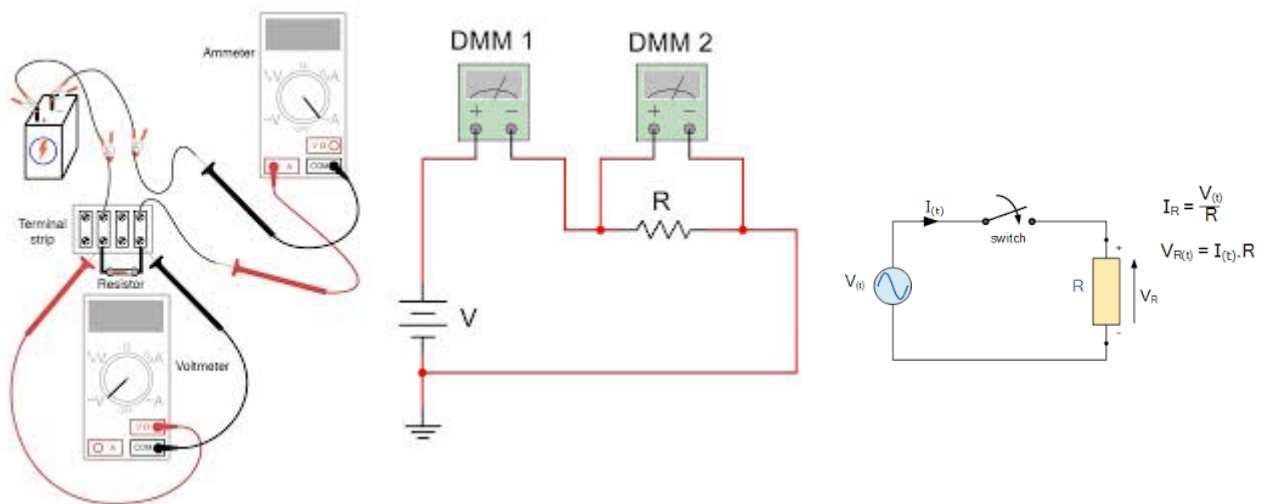**Schematic Diagram:** Source (DC/AC) → Resistor → Measurement Points (For AC, use a function generator; for DC, use a DC supply.)



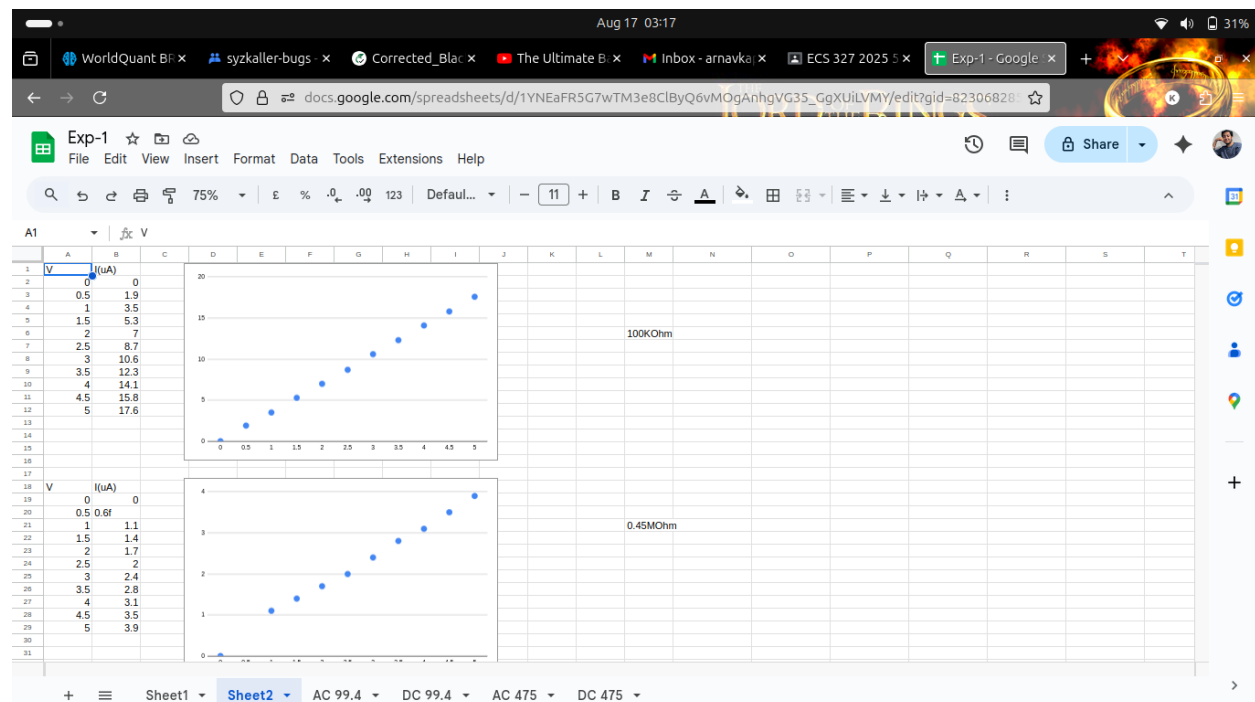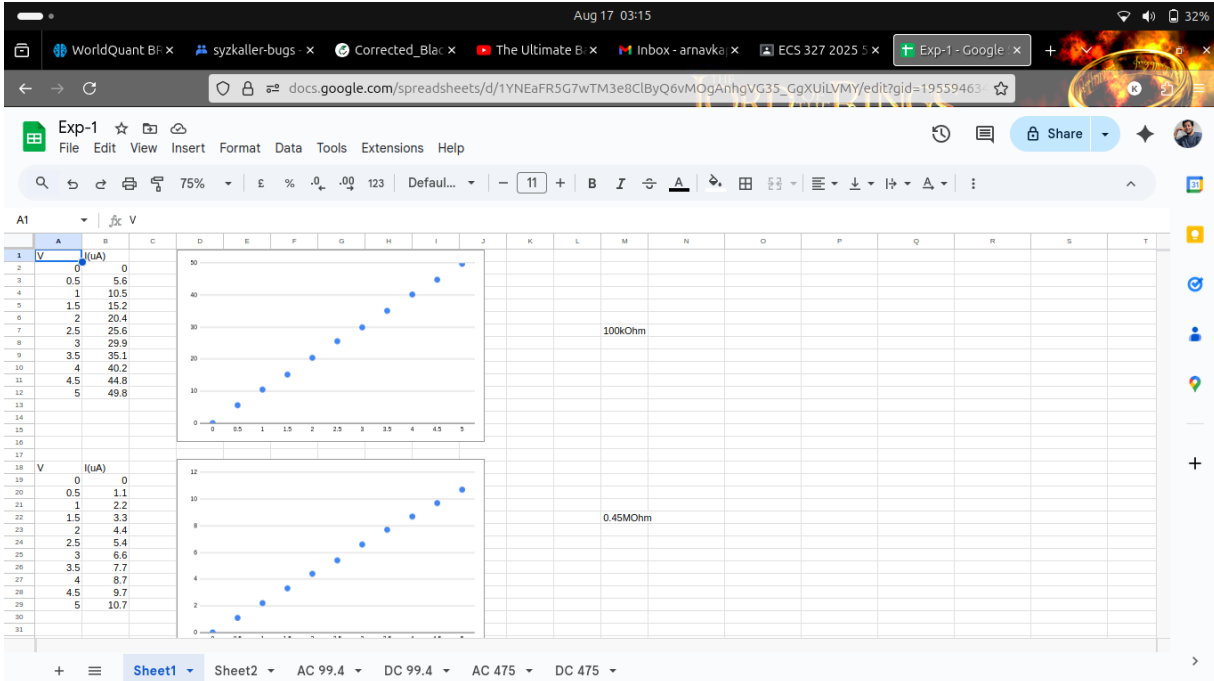**Results:** - DC V-I Characteristics: For each resistor, plot voltage (V) vs. current (I) using measured data from exp-1.xlsx. The slope of the V-I curve gives the resistance value. (See attached plots from exp-1.xlsx)



## **Discussion:** -

### **1. Calculate the slopes and justify your results.**

The slope of the V-I curve ( $\Delta V / \Delta I$ ) for each resistor should match its resistance value.

- DC Setup giving  $R1 = 100\text{k}\Omega$  and  $R2 = 0.45\text{M}\Omega$

- AC Setup giving  $R1 = 100\text{k}\Omega$  and  $R2 = 0.45\text{M}\Omega$

For ohmic resistors, the relationship is linear, confirming Ohm's Law ( $V = IR$ ). Any deviation may be due to measurement error or non-ideal behavior.

### **2. Explain the color code of a given resistor and calculate your resistance code (with tolerance and units).**

- 100 k $\Omega$  example:

A resistor with bands Brown, Black, Yellow, Gold has a value of 1 (Brown), 0 (Black), 4 zeros (Yellow) = 100,000  $\Omega$  (100 k $\Omega$ ) with  $\pm 5\%$  tolerance (Gold)  $\rightarrow$  range 95,000–105,000  $\Omega$ .

- 0.45 M $\Omega$  example:

A resistor with bands Yellow, Green, Yellow, Gold has a value of 4 (Yellow), 5 (Green), 4 zeros (Yellow) = 450,000  $\Omega$  (0.45 M $\Omega$ ) with  $\pm 5\%$  tolerance (Gold)  $\rightarrow$  range 427,500–472,500  $\Omega$ .

### **3. Explain the relation between $V_{ab}$ , $V_{cd}$ and $V_{ef}$ : $V_{ab} = V_{cd} - V_{ef} = 2V_{xyz}$**

This equation relates the measured voltages at different points in the circuit, showing how the total voltage is distributed across components.

### **4. What is “non-ohmic” behavior? Mention any non-ohmic device and explain shortly**

Non-ohmic behavior refers to devices whose V-I relationship is not linear (does not follow Ohm's Law). Example: A diode is non-ohmic; its current increases exponentially with voltage after a threshold, not linearly.

**Experimental Setup:**



